

EE 464
Static Power Conversion II
Simulation Project I

Ozan Can İYİER, Özgür ERTÜRK

March 2019



Introduction

In this simulation project, Cuk converter is investigated. For specified operating conditions, a Cuk converter is designed. The design specifications are as following;

- Input Voltage: 9 V
- Output Voltage: -12 V
- Output Current: 3 A
- Switching frequency: 100 kHz
- Output voltage ripple: 2%

After this design process, a buck-boost converter is also designed and simulated. The outputs of two converters are compared. At the last part of the project, we designed a controller for a variable input voltage in order to keep output voltage at desired value.

Part a

For desired Input-Output Voltage Relation; we set the duty cycle from following calculation.

$$\frac{V_{out}}{V_{in}} = \frac{9}{12} = \frac{D}{1-D}$$

$$D = 0.57$$

After this decision, we built the circuit in Simulink platform, which is indicated at Figure 1 and simulated for desired input and output parameters. According to simulation results, the inductor, capacitor and load values are determined

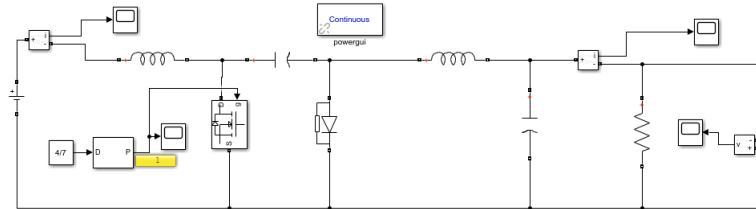


Figure 1: The Schematic of Cuk Converter

We choose capacitors as bulky as possible in order to provide a proper operation. The following values are determined for components;

Table 1: Component List

Component	Value
Inductor 1	4.7 mH
Inductor 2	4.7 mH
Capacitor 1	100 μ F
Capacitor 2	1 mF
Load	4 Ω

**Inductor 1 and Capacitor 1 are the ones stay at left side of the schematic.*

After selection of components and simulating the overall circuit, we have obtained the following voltage current waveforms and statistics.



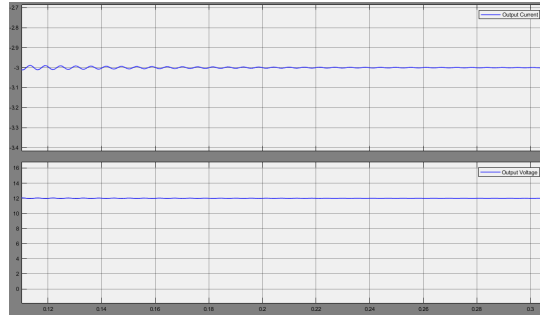


Figure 2: Output Current and Voltage Waveforms

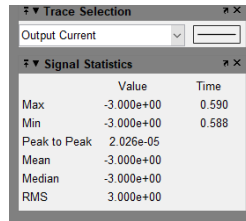

(a) Output Current Statistics

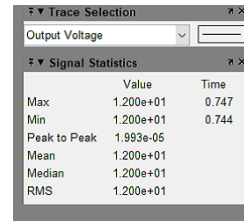

(b) Output Voltage Statistics

Part b

The buck-boost converter with similar operating conditions is designed. The schematic can be seen from Figure 4.

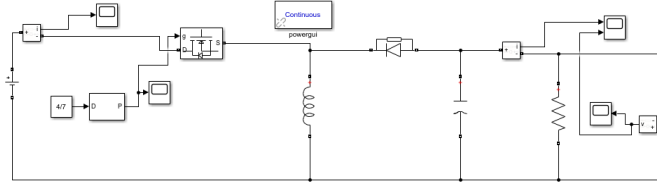


Figure 4: The Schematic of Buck-Boost Converter

After simulating the both Cuk and Buck-Boost Converters, we have obtained the following input current characteristics.

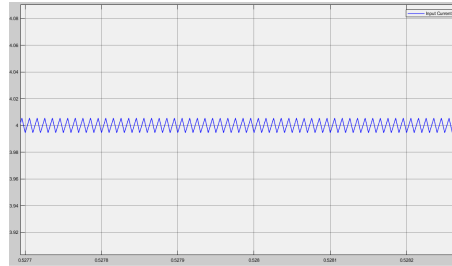


Figure 5: The Input Current Waveform of Cuk Converter

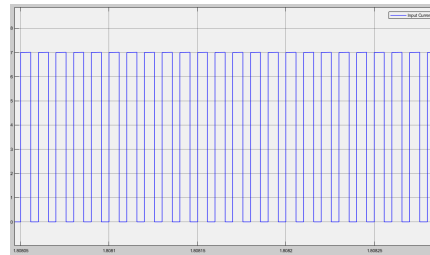


Figure 6: The Input Current Waveform of Buck-Boost Converter

From the waveforms and statistics, we can state that the input current of Buck-Boost Converter has much rippled characteristics than Cuk converter. Because Cuk converter includes two inductors and two capacitors, the input current is more continuous than Buck-Boost converter. In addition, the average value of Cuk Converter's input current is higher than buck-boost. The peak value of Buck-Boost converter's input current is higher than Cuk Converter's. This can be some extra stress on switching device unless some protective devices are used such as snubber etc.

Value	Time
Max 4.005e+00	0.663
Min 3.995e+00	0.662
Peak to Peak 1.094e-02	
Mean 4.003e+00	
Median 4.005e+00	
RMS 4.003e+00	

(a) Cuk Converter Input Current Statistics

Value	Time
Max 7.005e+00	1.808
Min 2.099e-08	1.808
Peak to Peak 7.005e+00	
Mean 1.667e+00	
Median 2.099e-08	
RMS 3.417e+00	

(b) Buck-Boost Input Current Statistics

Part c

The following equations are defines the ripple values of the inductor and capacitor;

$$\Delta i_{L_1} = \frac{V_C - V_{in}}{L_1} * (1 - D) * T_s = \frac{21 - 9}{4.7 * 10^{-3}} * (1 - 0.57) * \frac{1}{100000} = 0.011A$$

$$\Delta i_{L_2} = \frac{V_{out}}{L_2} * (1 - D) * T_s = \frac{12}{4.7 * 10^{-3}} * (1 - 0.57) * \frac{1}{100000} = 0.011A$$

*Assumed i_{L_1} is constant.

$$\Delta V_{C_1} = \frac{i_{L_2}}{C_1} * (1 - D) * T_s = \frac{3}{100 * 10^{-6}} * (1 - 0.57) * \frac{1}{100000} = 0.119V$$

The results are consistent with the findings.

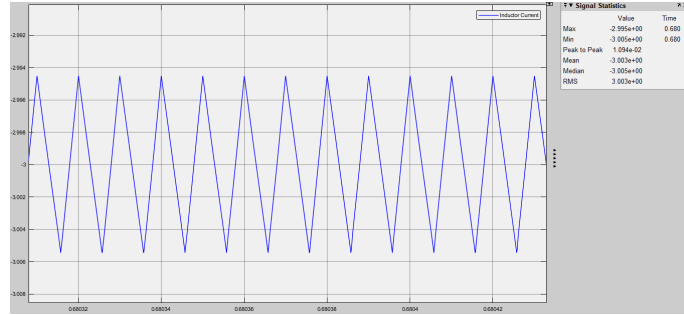


Figure 8: The Inductor Current Waveform

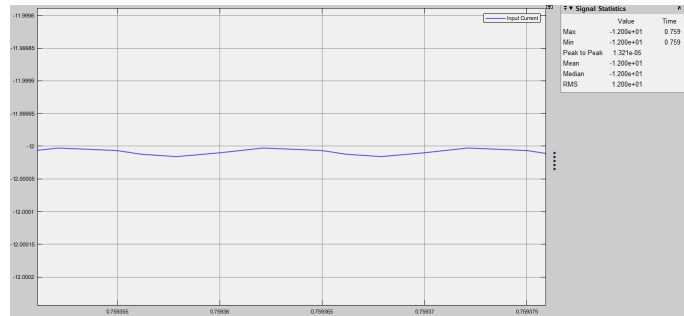


Figure 9: The Capacitor Voltage Waveform

Part d

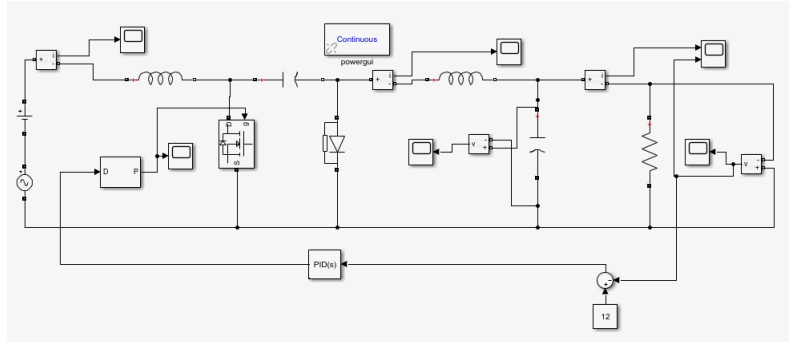


Figure 10: Circuit Schematic of the PI Controlled Converter

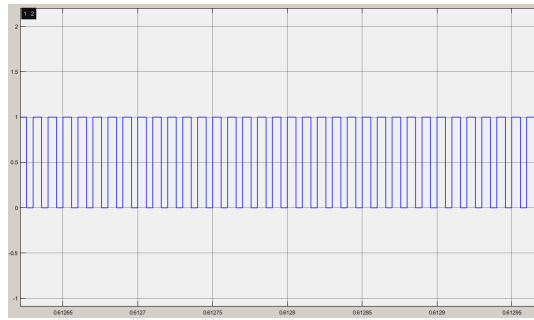


Figure 11: Duty Cycle Variation

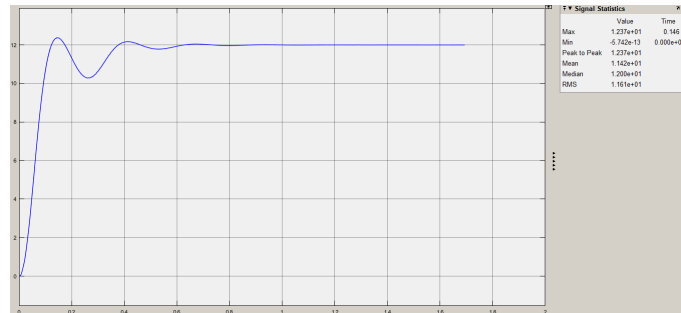


Figure 12: Output Voltage

We used a PI controller, the parameters of the controller is indicated at following figure 13, to calculate and cancel out the error in time as P controller is not capable of cancelling out the error completely. We measured the output voltage and subtracted it from the wanted 12 Voltage and gave it to the PI controller block built-in in the Simulink libraries.

From the Figure 12, we see that 2 percent settling time is approximately equal to 0.6 seconds.

Controller parameters	
Source:	Internal
Proportional (P):	0.055
Integral (I):	0.6
Derivative (D):	0
Filter coefficient (N):	100
Select Tuning Method:	Transfer Function Based (PID Tuner App) Tune...

Figure 13: PID Parameters

Part e

We changed the input voltage and run the simulation again and saw that almost nothing changed, even the settling time.

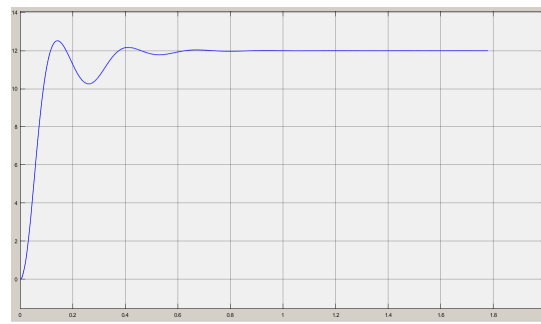


Figure 14: Output Voltage

Input change does not change anything in our controller's operating system, so it is understandable that not much has changed, however we expected some changes in the settling time or peak time of the response of the circuit but as it can be seen here nearly nothing changed in the response graph.